

ECE2810 Digital Systems Design Laboratory

Laboratory Report #2

Name:

Student ID:

Date:

2025-9-26

The Chinese University of Hong Kong, Shenzhen


- Experiment A: Using Logic Analyzer
- Experiment B: Guided Multisim Simulation
- Experiment C: Individual Gate Test (Hardware Experiment)
- Experiment D: Combination of Gates (Simulation and Hardware Experiment)

1. Experiment A


Learn how to use the logic analyzer!


2. Experiment B

2.1 Design

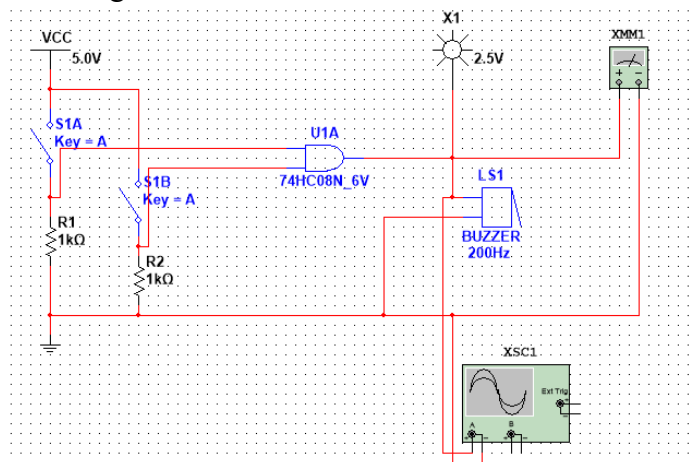

2.11 Result

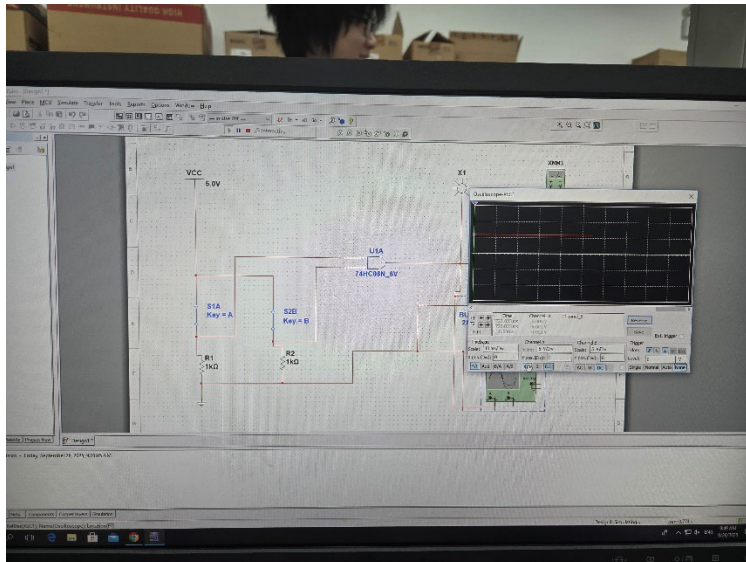

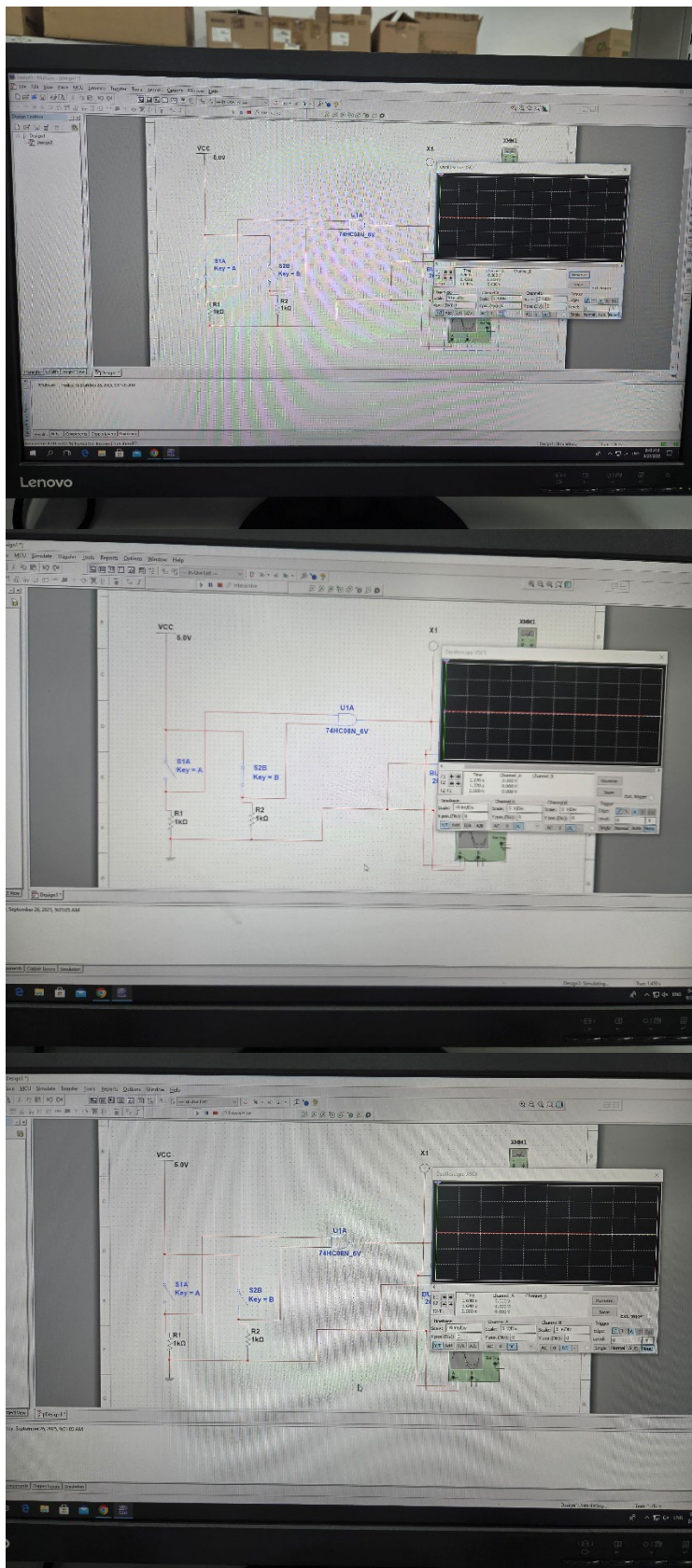

Learn how to use software to simulate the behaviors of circuit designs and function

3 Experiment C

Results:

NAND GATE

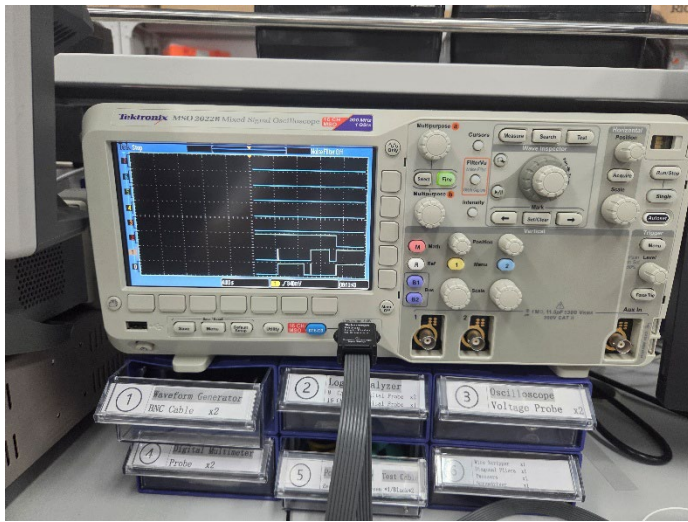


Table 1

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

OR GATE

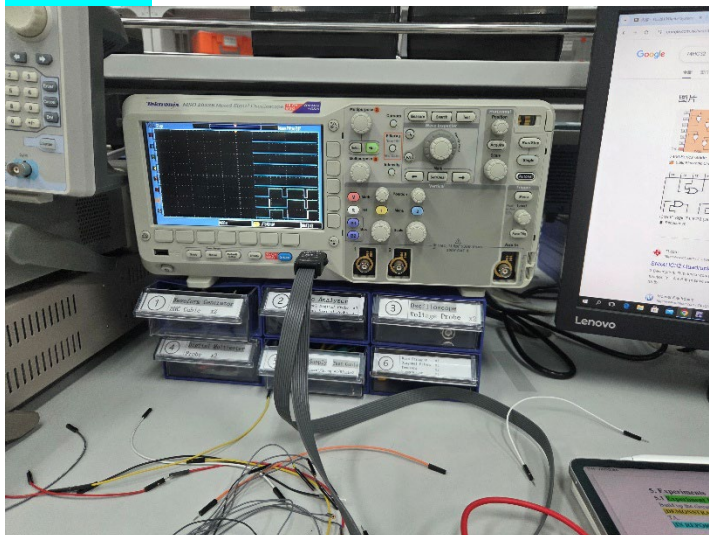


Table 3

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

XOR GATE

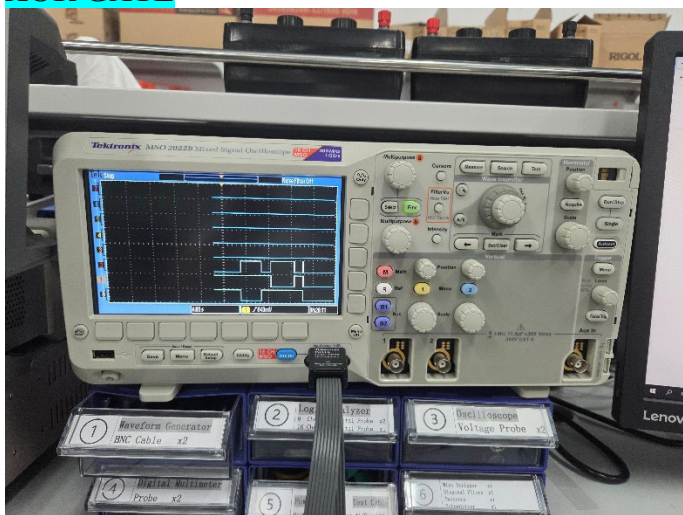


Table 4

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XNOR GATE



Table 5

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

NOR GATE


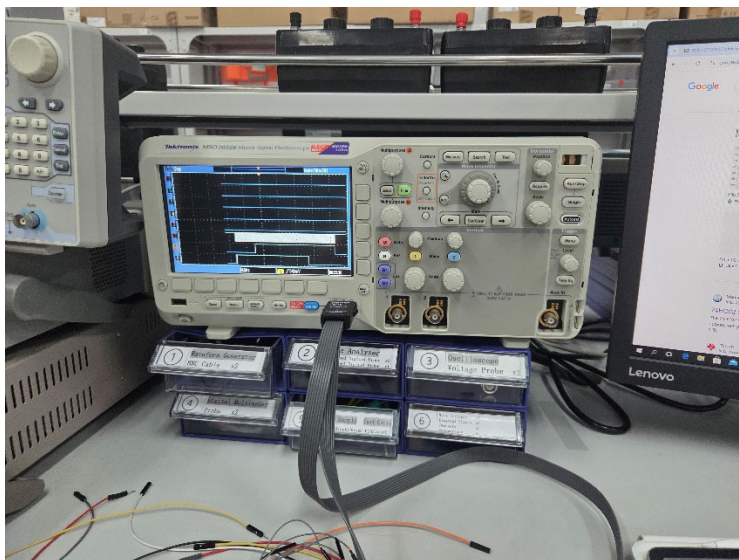
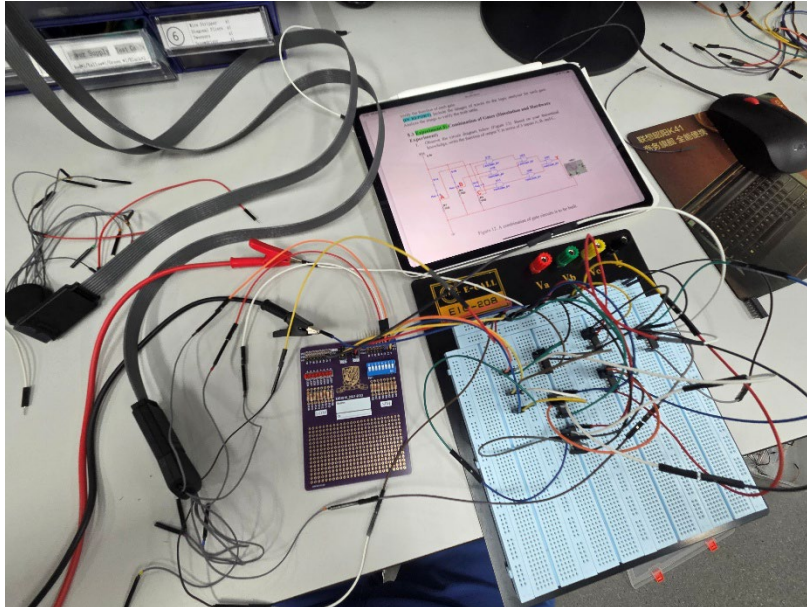


Table 2

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


4 Experiment D




4.1 Design

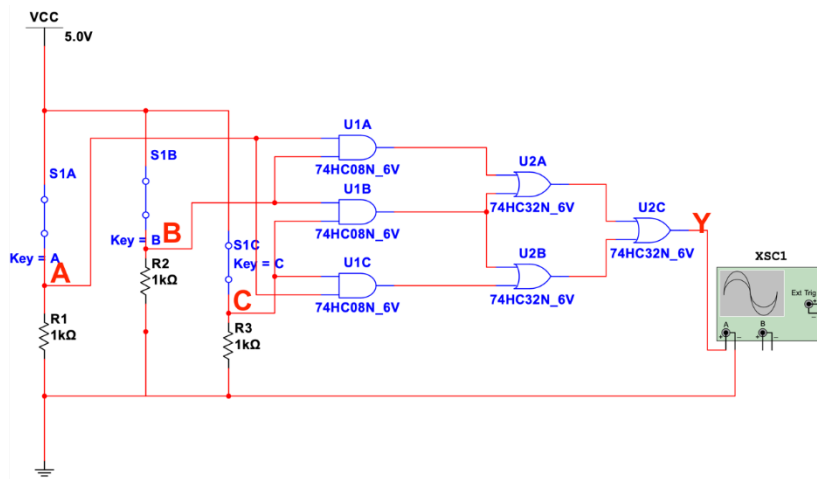

4.2 Results:

$Y = AB + BC + AC$

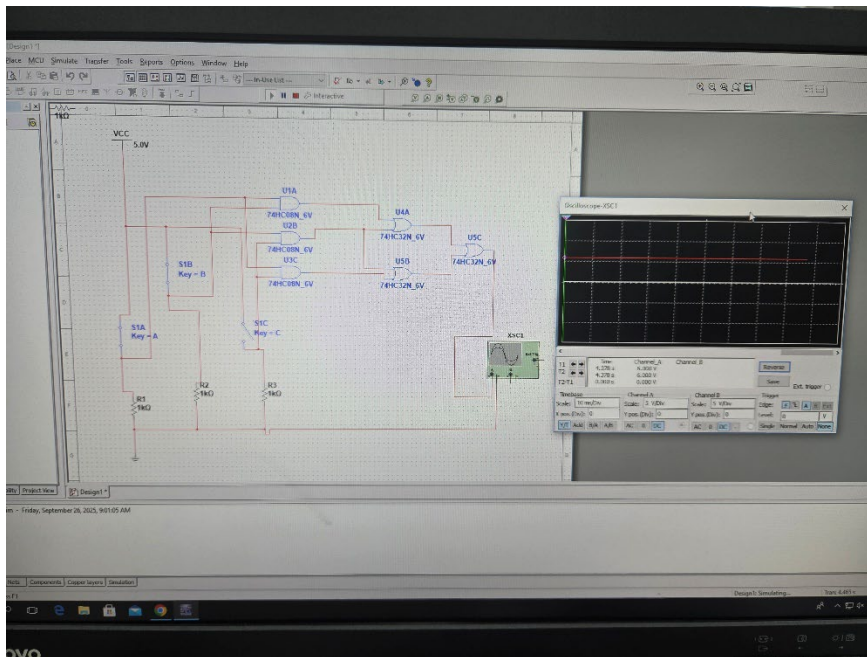

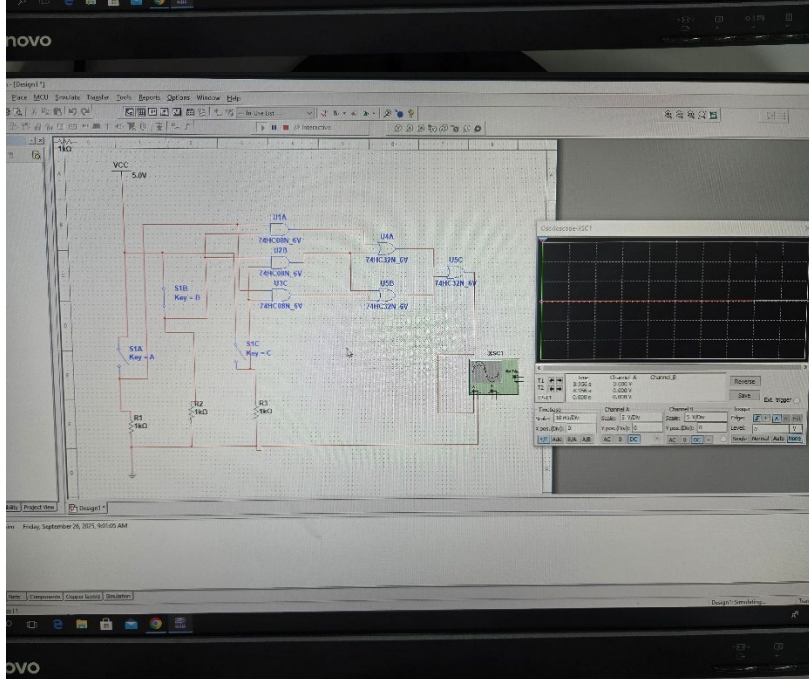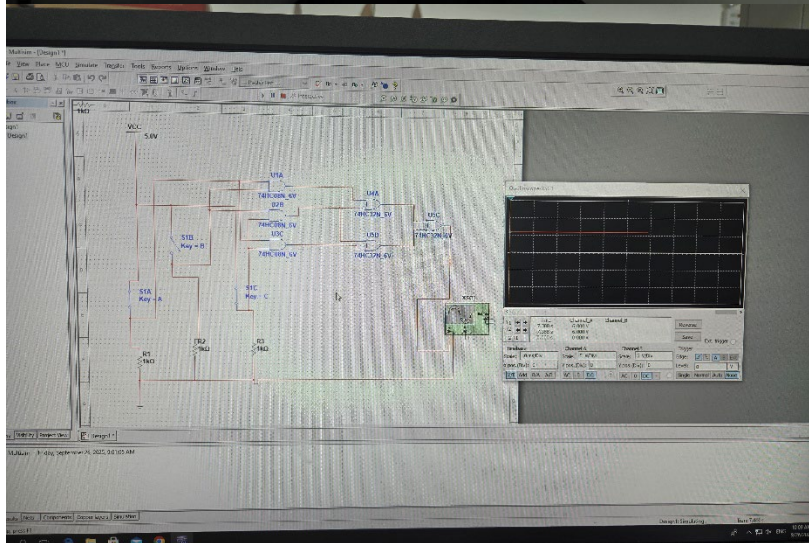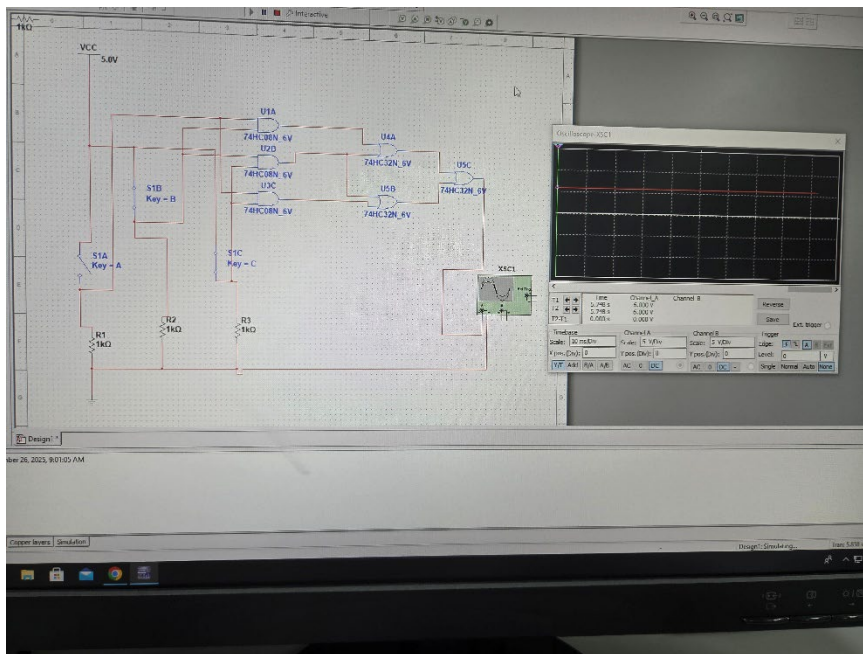


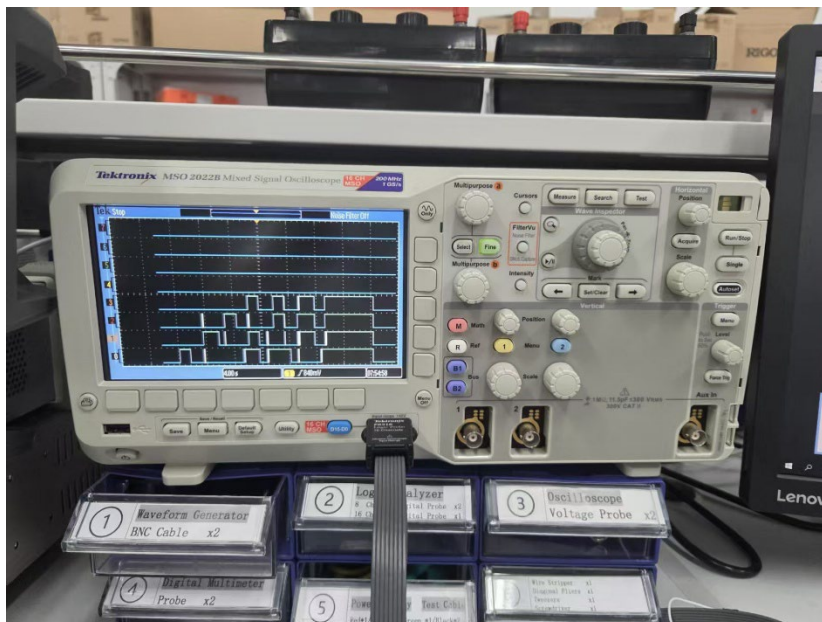


Table 6

A	B	C	Y
0	0	0	0
1	0	0	0
0	1	0	0
0	0	1	0
1	1	0	1
1	0	1	1
0	1	1	1
1	1	1	1

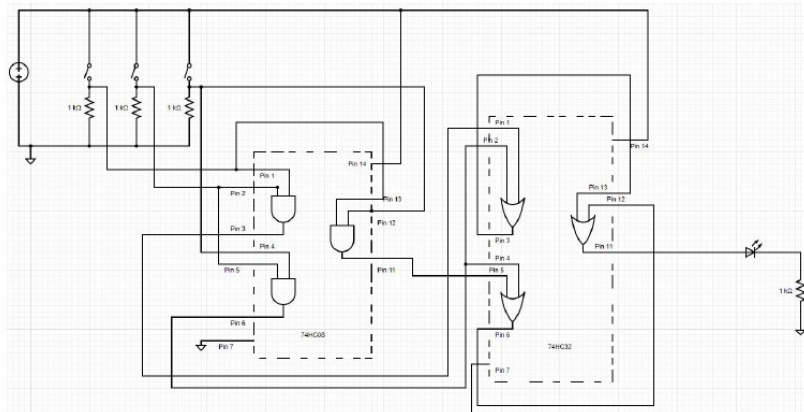

4.3 Questions

I think it could be kind of design of Traffic Light.

Conclusion

In this lab, we learned how to use Multisim, verified the logic function of NAND Gate, NOR Gate, OR Gate, XOR Gate, and XNOR Gate, verified the functional completeness of NAND Gate, and used NAND Gates to construct AND Gate, NOT Gate, OR Gate, NOR Gate, XOR Gate, and XNOR Gate, simulated and realized a complex logic using the combination of the Gates. From the lab, we know:

- 1) The way to use Multisim
- 2) The way to construct a Gate with other kinds of Gates
- 3) NAND Gates have the property of functional completeness
- 4) The way to construct a complex logic with several kinds of Gates.